

Date : 27 May
Course : logic design.
Repository : Rashmi.k

Name : Rashmi
USN : 4AL18EC043
Sem : IV Sem.

Report :

Boolean algebra -

It is defined with set of elements, a set of operators & a number of axioms / postulates.

set of elements (b.i)

set of operation : AND, OR

AND

OR

$$0 \cdot 0 = 0$$

$$0 + 0 = 0$$

$$0 \cdot 1 = 0$$

$$0 + 1 = 1$$

$$1 \cdot 0 = 0$$

$$1 + 0 = 1$$

$$1 \cdot 1 = 1$$

$$1 + 1 = 1$$

The additive identity - 0

The multiplication identity - 1

laws of Boolean algebra

1) Commutative law - $A + B = B + A$

2) Associative law - $x + (y + z) = (x + y) + z$

3) Distributive law - $x(y + z) = (xy) + (xz)$


Theorem :

1) Absorption theorem - $x + xy = x$

NOT to logic gates :

NAND, NOR - Universal gates.

Universal logic

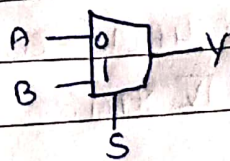


$$2^n = 1$$

$$2^n = \text{inputs}$$

$$n = \text{selection lines}$$

inverter design :

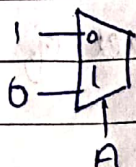

$$Y = 1 \cdot \bar{A} + 0 \cdot A$$

$$Y = \bar{A}$$

$$Y = A\bar{S} + BS$$

$$\text{OR} - A + B$$

$$\text{Ex-OR} - A \oplus B$$

$$\text{Ex-NOR} - A \odot B$$

$$\text{AND} - A \cdot B$$

BCD to 7 segment decoder :

